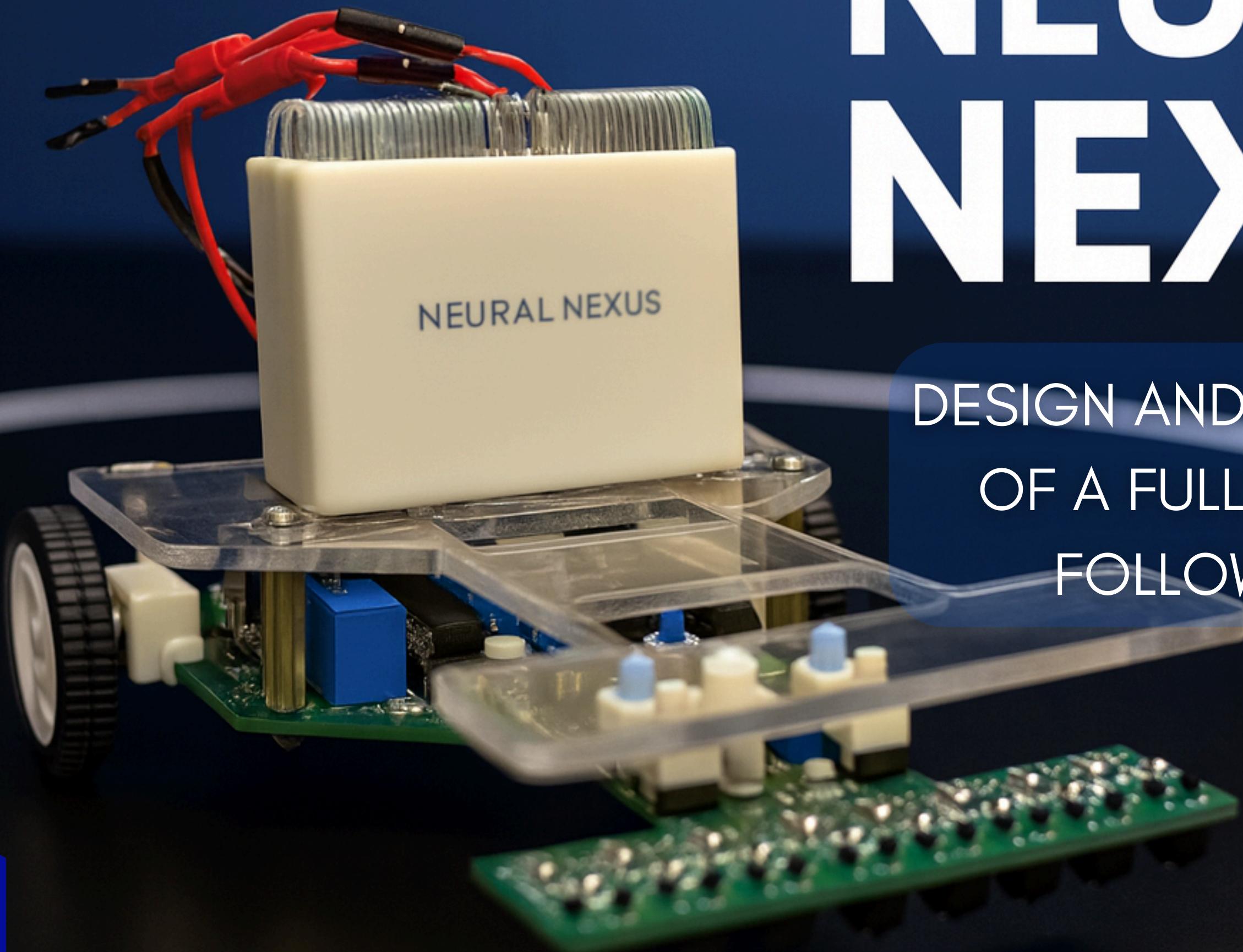





EN2091 - LABORATORY PRACTICE
AND PROJECTS



NEURAL NEXUS

DESIGN AND IMPLEMENTATION
OF A FULLY ANALOG LINE
FOLLOWING ROBOT

FLOW DIAGRAM

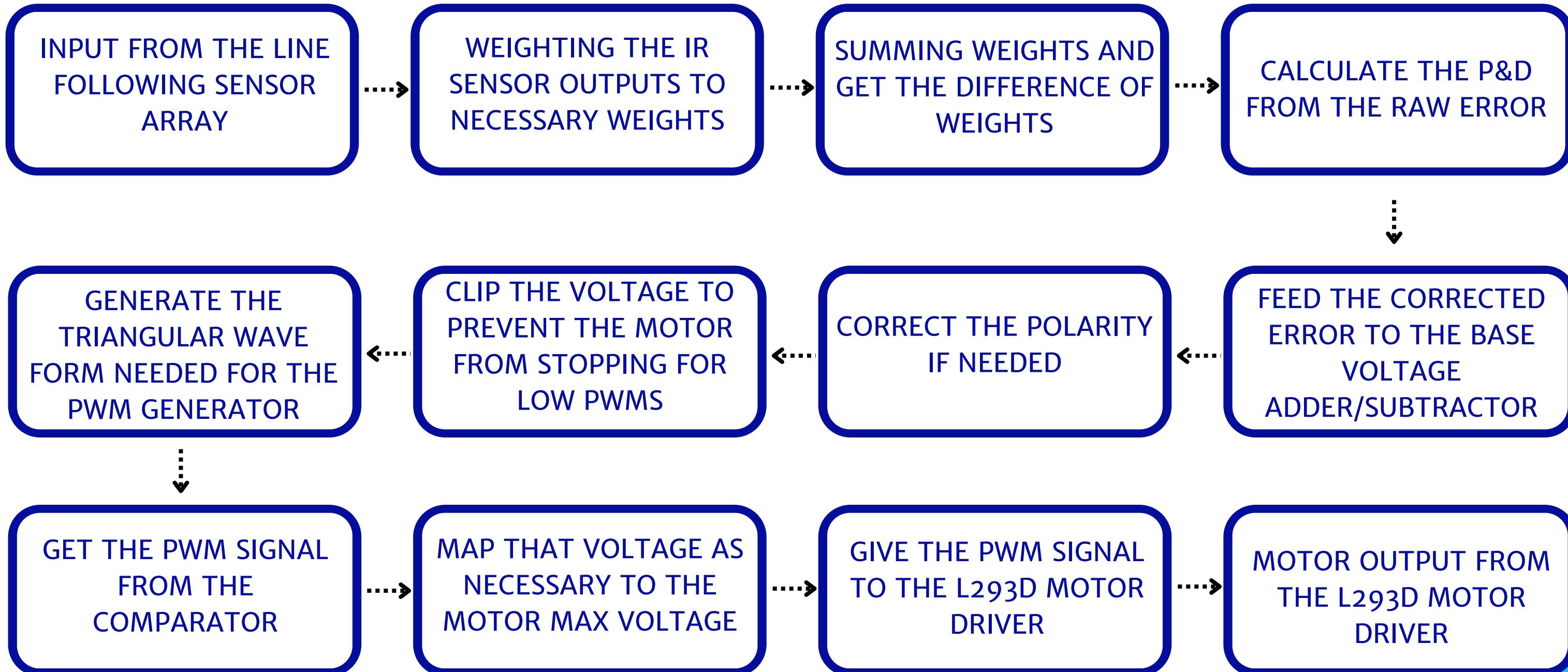


SENSOR ARRAY

- We are using TCRT5000 IR emitter and receiver to detect the line and we are getting the analog read from that sensor.
- We are using LM324 Quad Opamp IC.
- Low-cost and readily available: The LM324 is inexpensive, easy to source, and provides four op-amps in one package, reducing both cost and space in our design.
- LM324 (Slew rate 0.5V/us) 0–5V 10us.

PD CONTROL SYSTEM


- We are passing the weighted raw error to the PD Control system.
- We don't use I term here because The robot is constantly moving, so there's no steady state error to correct.
- In here we Mean by the steady state error is the small remaining error that stays even after the system stops changing.
- We adjust K_p by changing the amplification of the opamp amplifier.
- We adjust K_d by changing the resistance of the opamp differentiator.

SENSOR PANEL

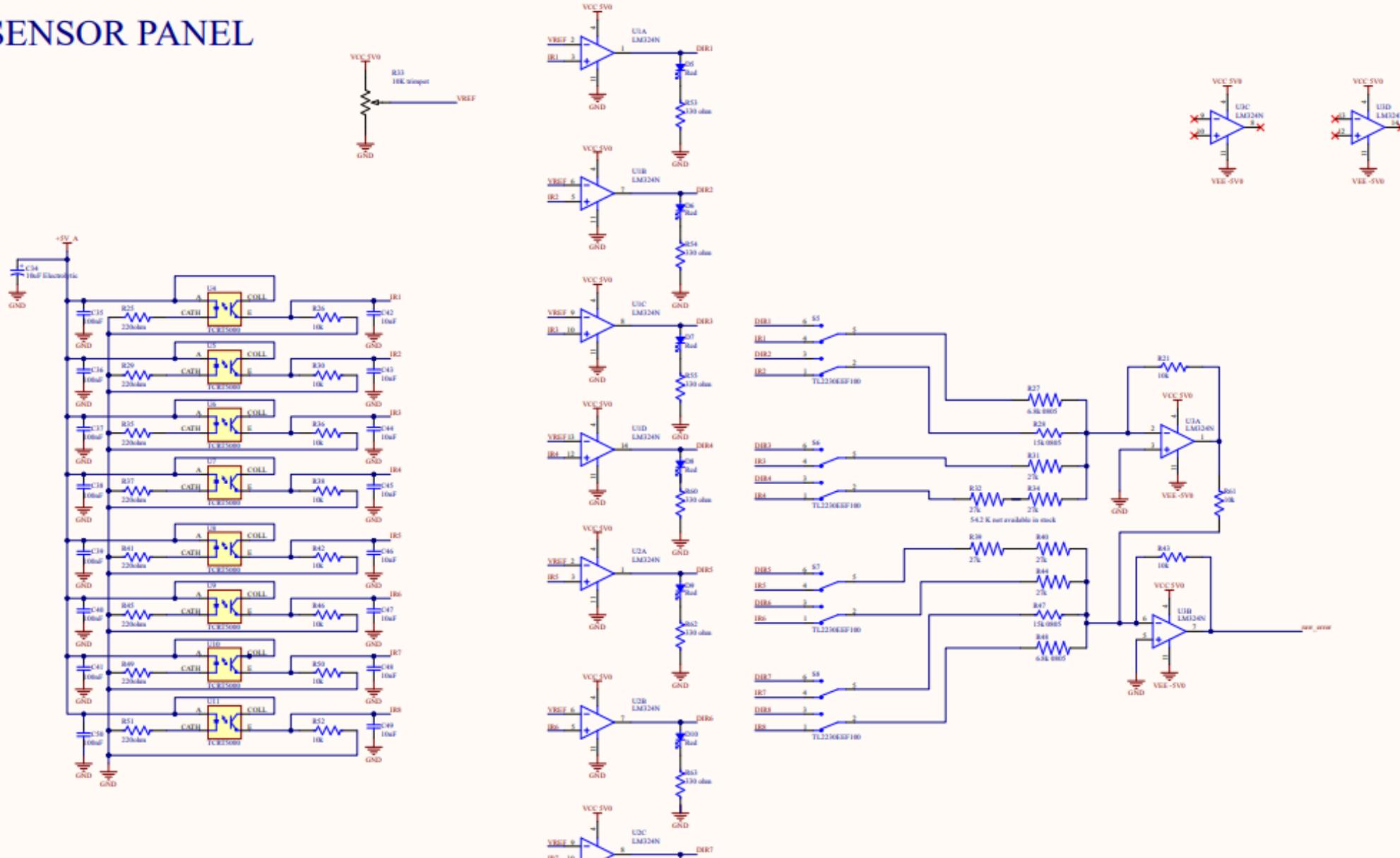

PD CONTROL SYSTEM

SENSOR ARRAY

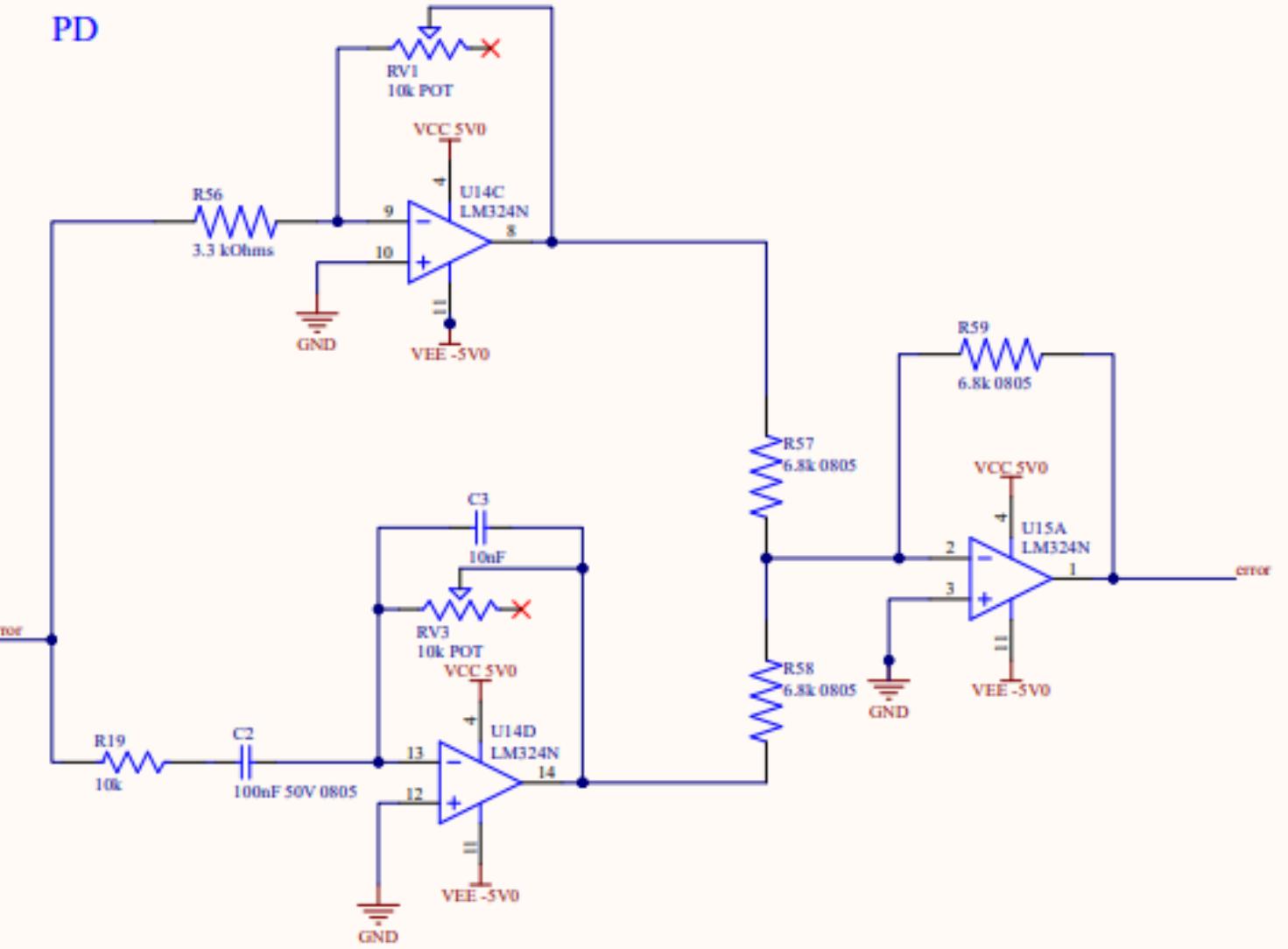

PWM SIGNAL GENERATOR


- This circuit generates the left and right PWM signals to control motor speeds through L293D motor driver.
- The error and base signals are processed by opamp stages to produce control voltages proportional to line deviation, so from the beginning we are using 2 lines as $V_b+error$ and $V_b-error$ and generate 2 PWM signals.
- Then we clip down that signal to avoid lower signals which make the wheels not to rotate for low PWM signals.
- These voltages are compared with a triangular waveform to create PWM signals.
- The PWM duty cycle changes according to the PD control output, allowing smooth and accurate steering correction.

Our robot's special features:


1. Adjustable PWM frequency
2. Adjustable base voltage of motors
3. Adjustable minimum clipping voltage (change the minimum speed of the motor)

PWM SIGNAL GENERATOR


TRIANGULAR WAVEFORM GENERATOR

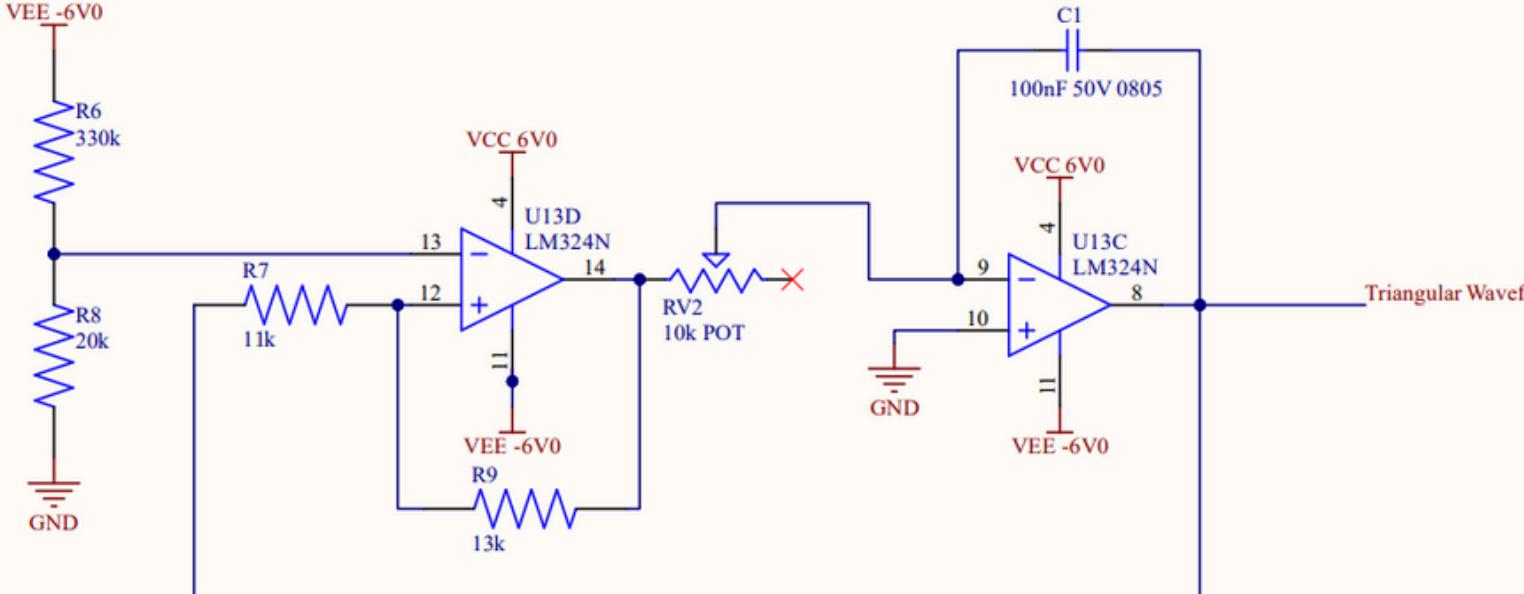


LEFT PWM

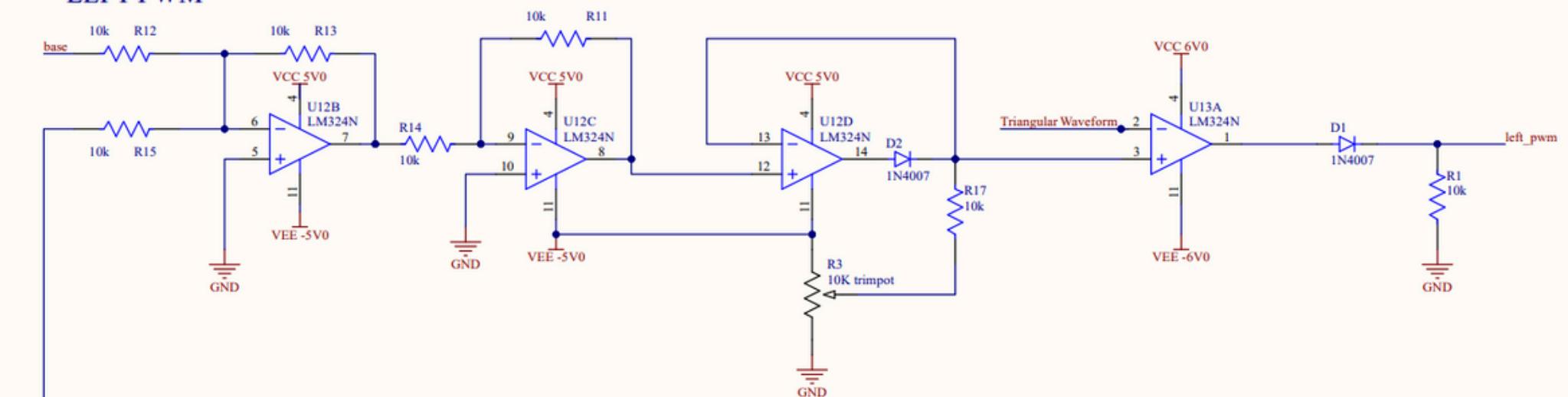


RIGHT PWM

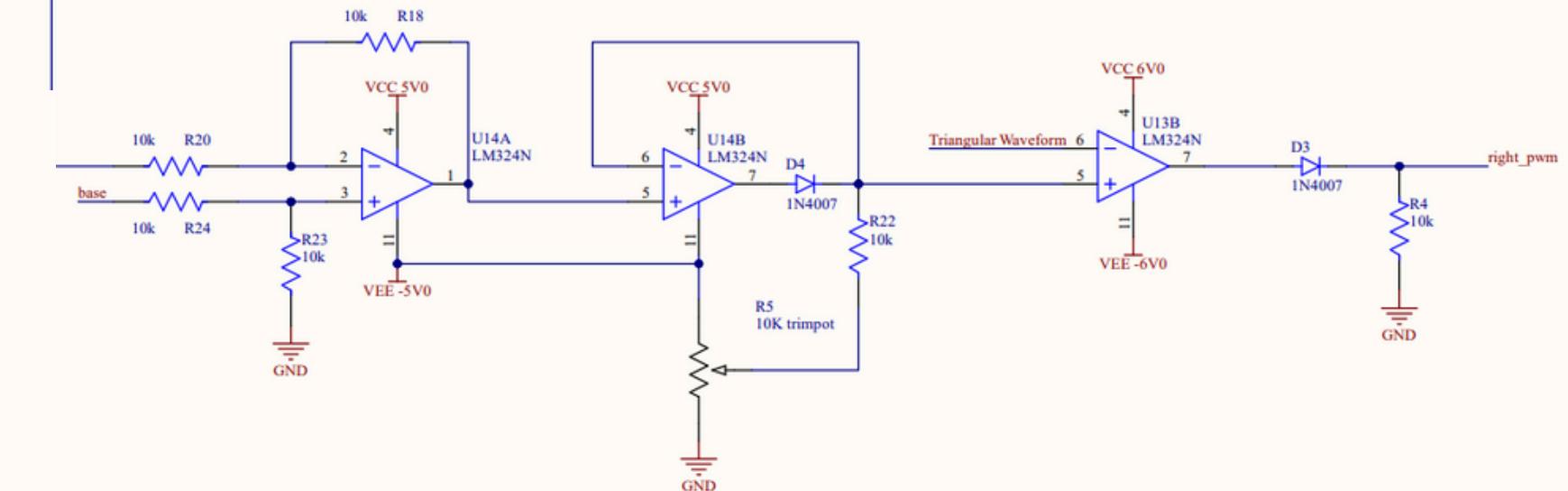


POWER DISTRIBUTION

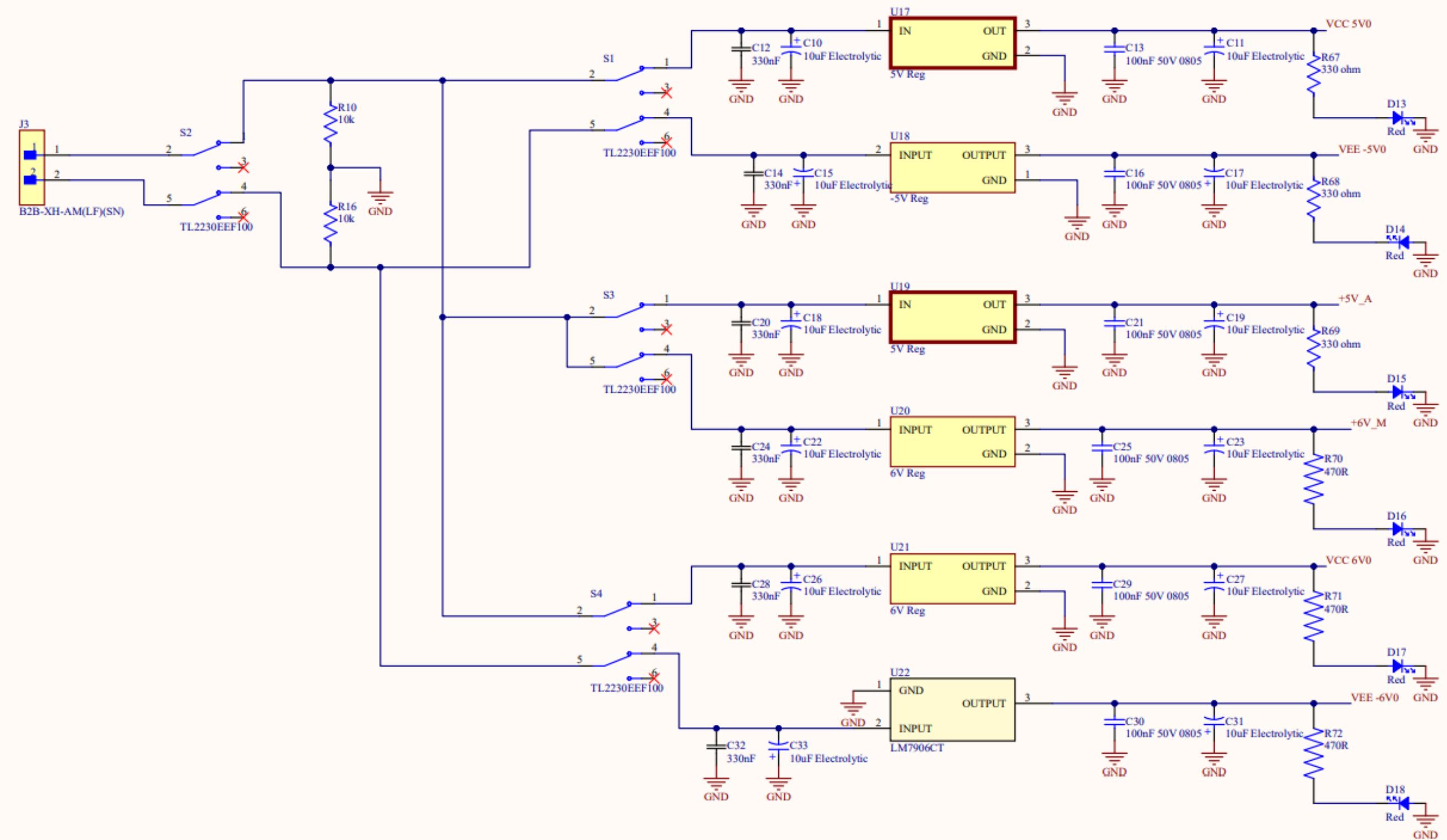


LT SPICE SIMULATION

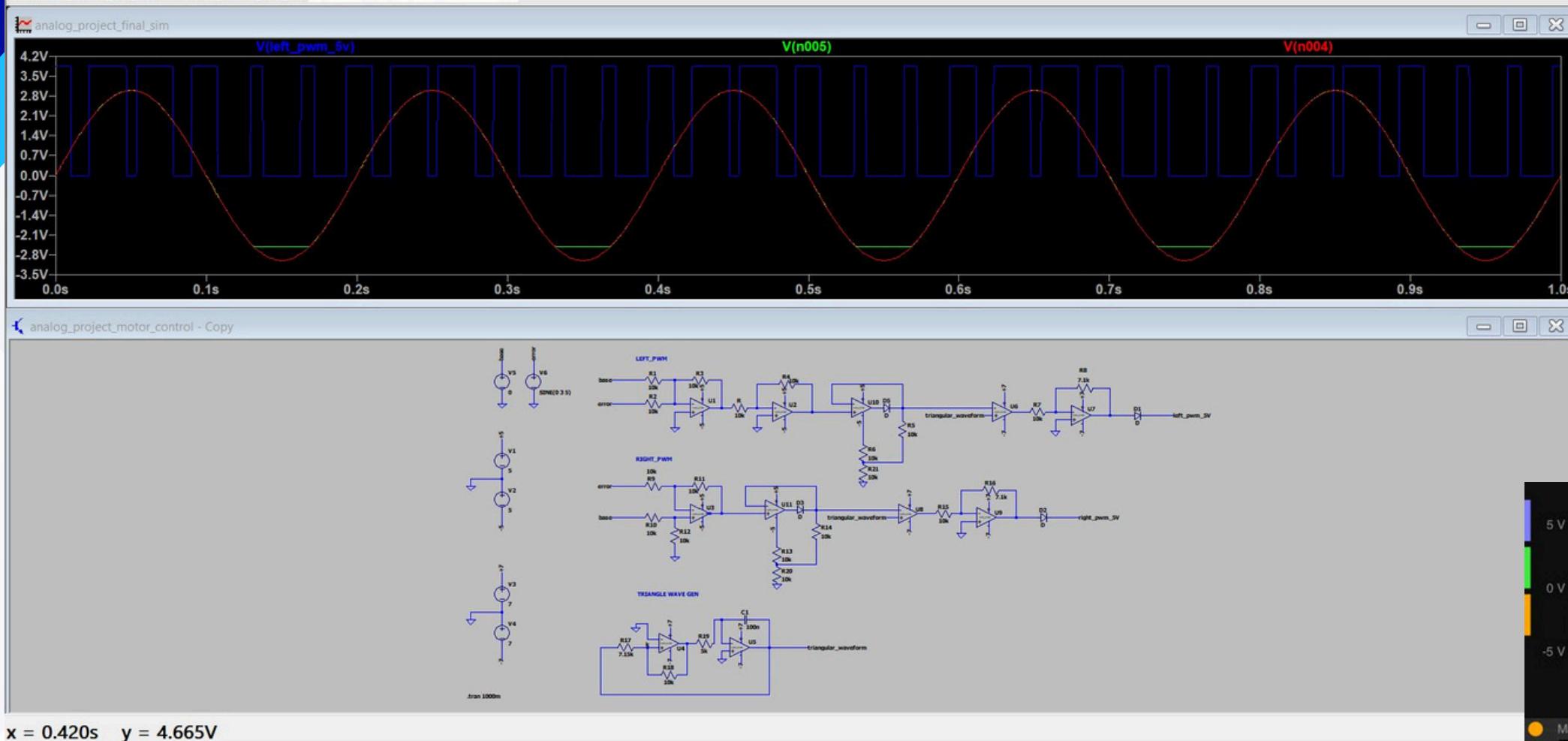


EVERYCIRCUIT SIMULATION

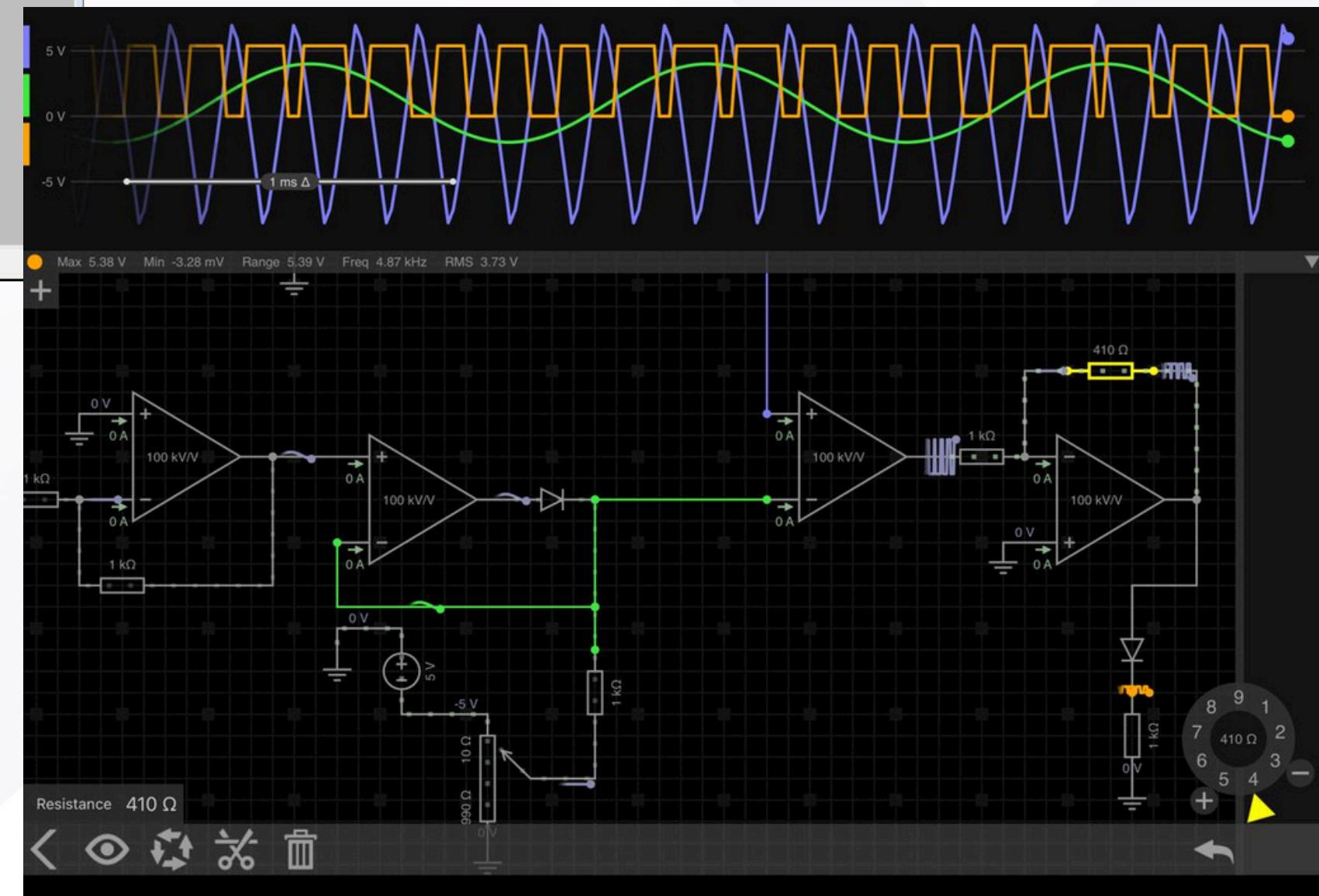


BREADBOARD IMPLEMENTATION

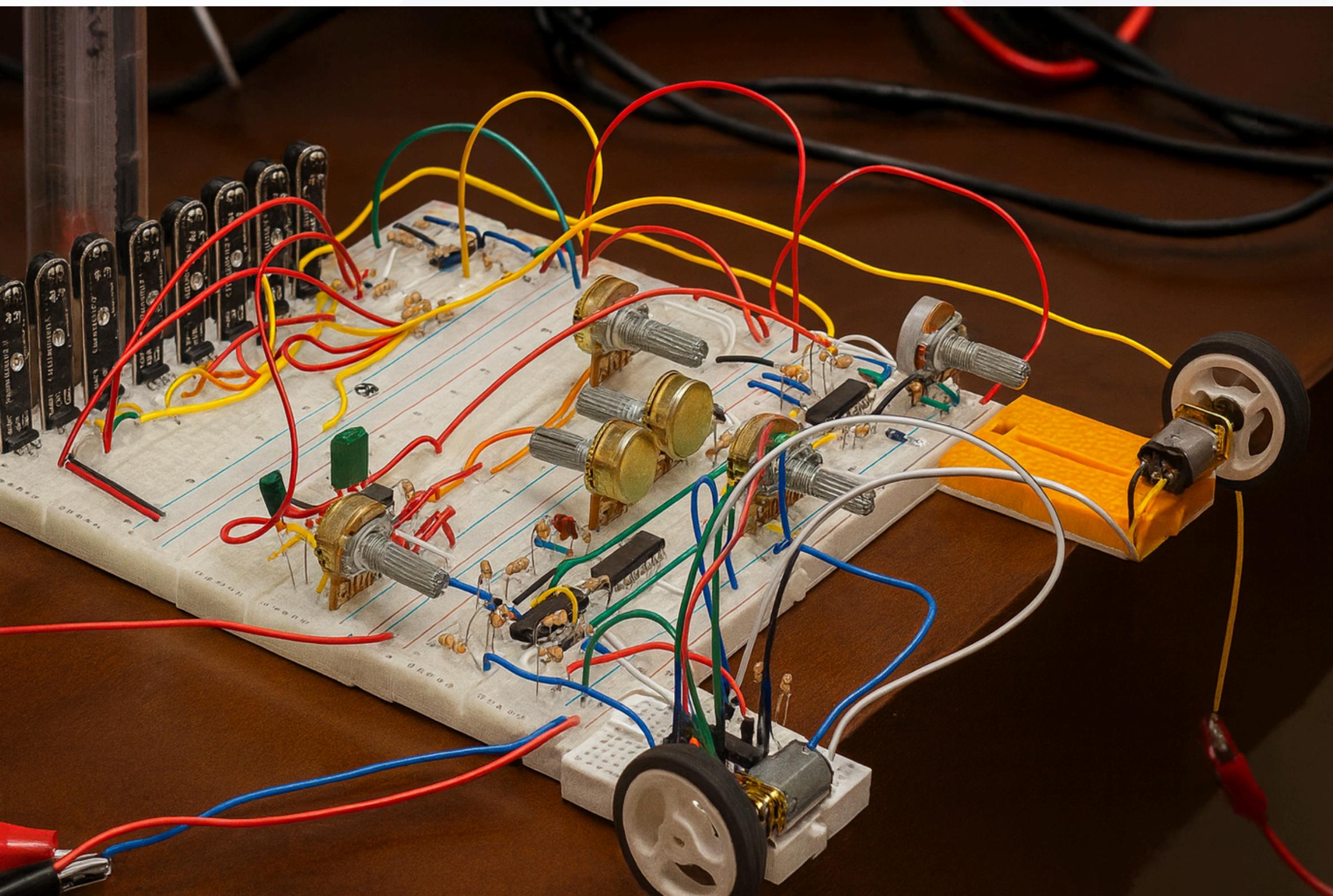

FINAL BREADBOARD IMPLEMENTATION

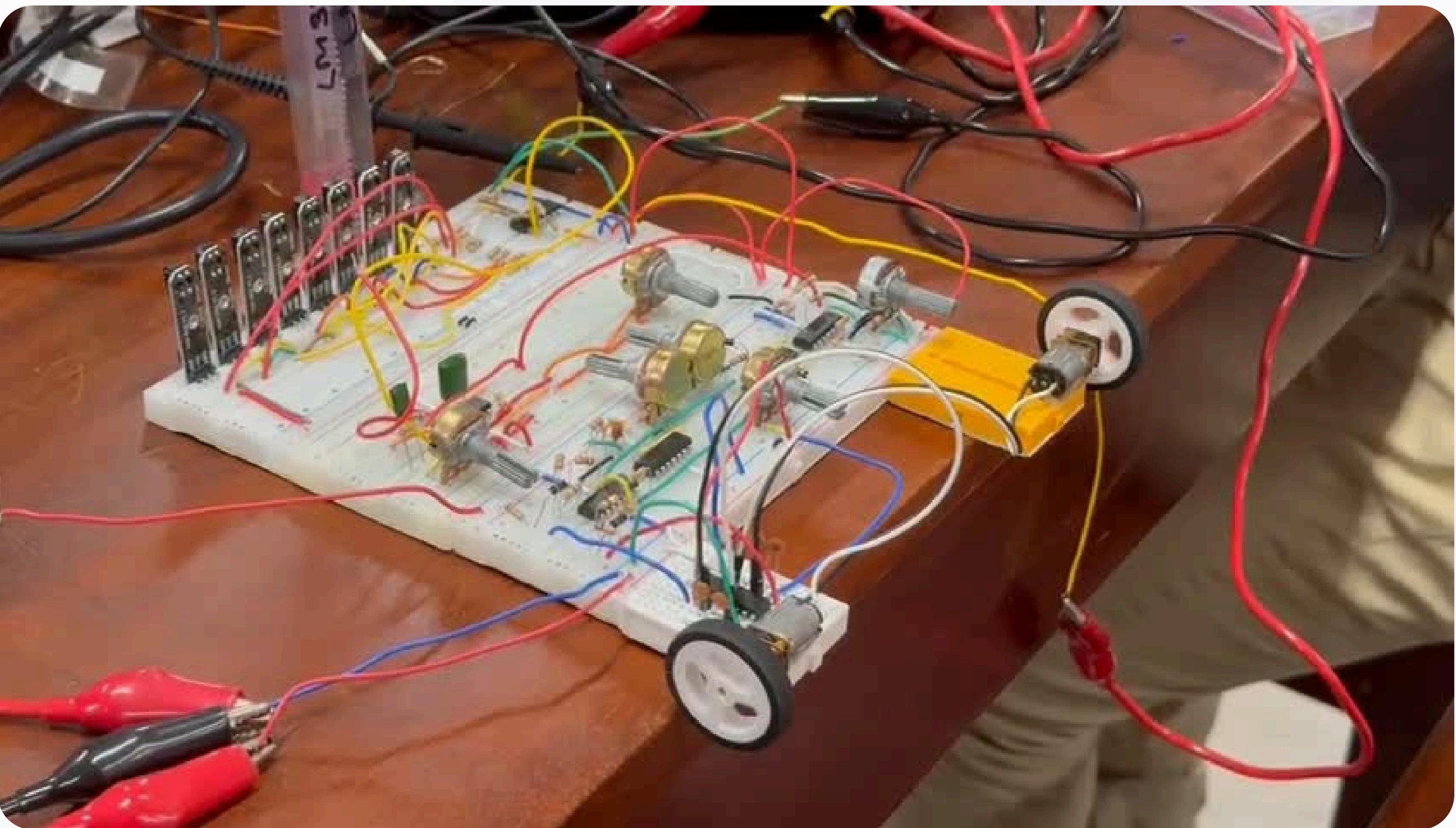

PCB DESIGN

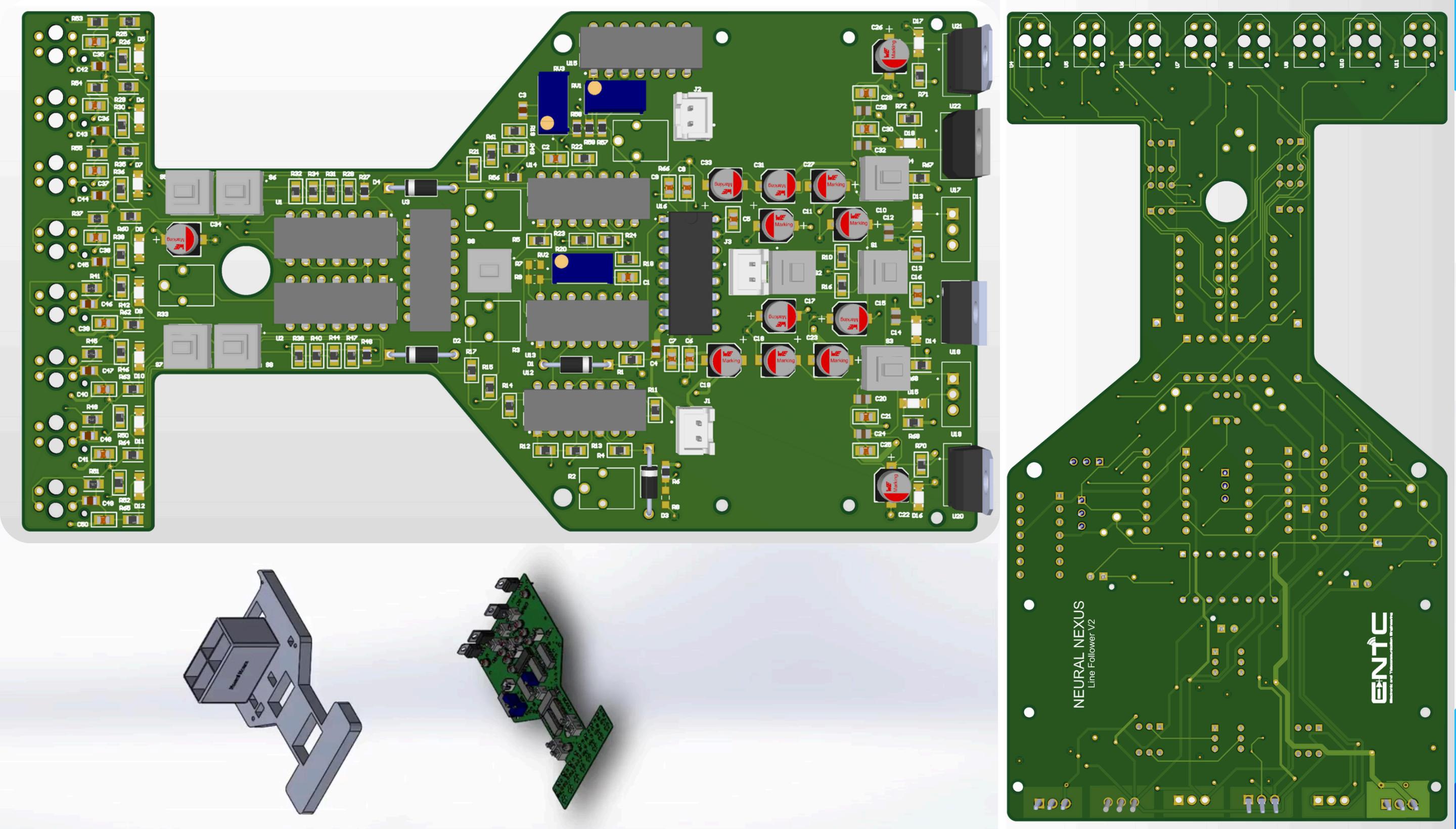

POWER BUDGET CALCULATION

	A	B	C	D	E
1	Item	Voltage (V)	Current (A)	Power (W)	Datasheets
2	Motor L (avg)	6	0.3	1.8	https://www.pololu.com/product/2368
3	Motor R (avg)	6	0.3	1.8	https://www.pololu.com/product/2368
4	Motors driver loss (total motors)	6	0.552	3.31	https://www.st.com/resource/en/datasheet/l293d.pdf
5	TCRT5000 IR LEDs (8)	5	0.144	0.72	https://www.vishay.com/docs/83760/tcrc5000.pdf
6	Op-amps + Misc analog	5	0.22	1.1	https://www.ti.com/lit/ds/symlink/lm324.pdf
7	Total System (approx)	7.4	0.75	5.6	
8					
9					
10					
11					
12	Battery Capacity (mAh)	Battery Capacity (Ah)	Total Draw (A)	Runtime (hours)	Runtime (minutes)
13	800	0.8	0.743	1.076716016	64.60296097
14					


USER INPUT CONTROLS

Left wheel minimum speed

Base speed

Triangular wave frequency

Motors/Sensor Array power supply

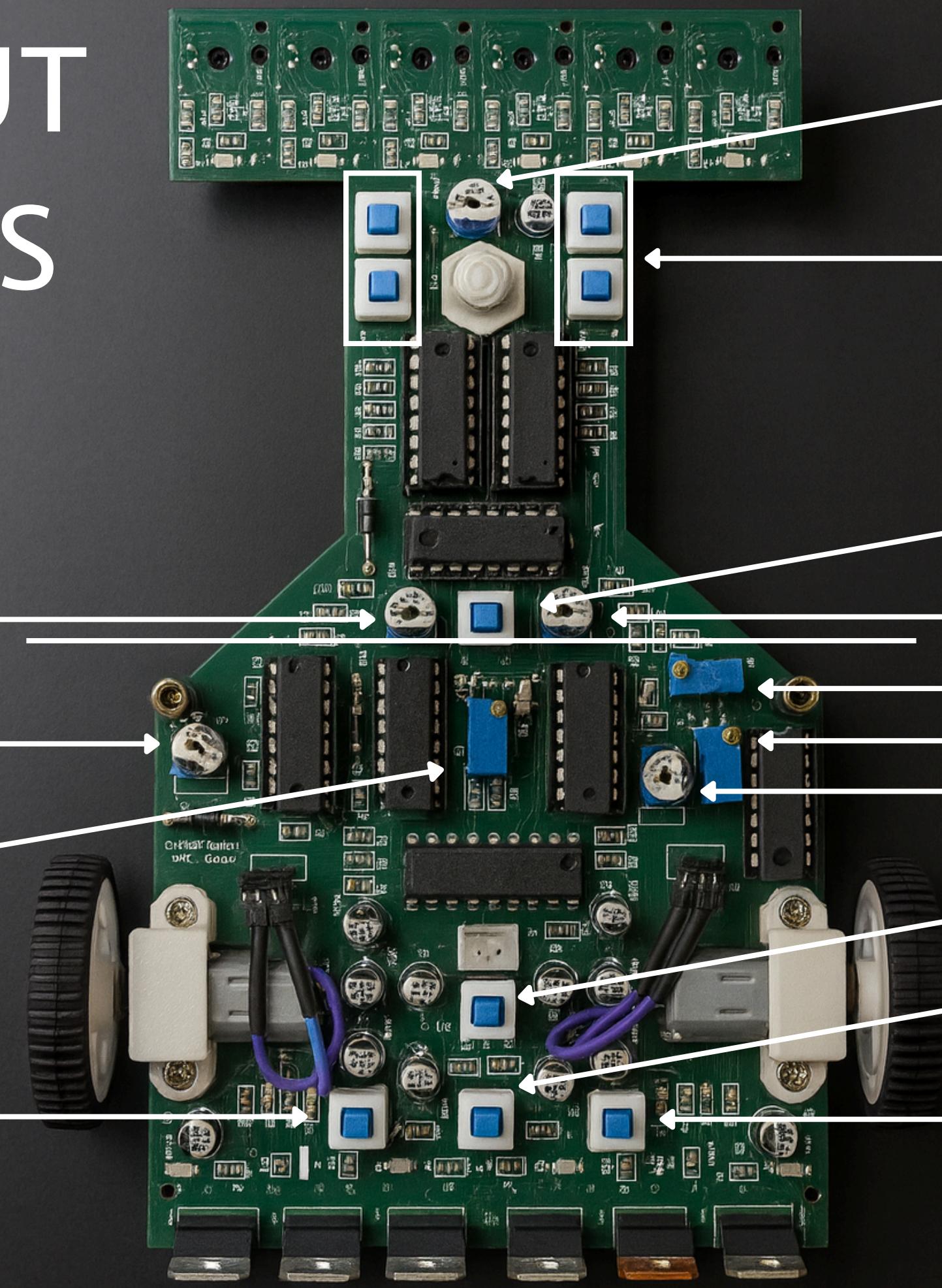

IR threshold

Digital & Analog conversion

Zero error switch

Right wheel minimum speed

Kd

Kp

Logic Level



Adjustement

Power ON/OFF

Regulated +5V/-5V

Regulated +6V/-6V

FINAL PRODUCT

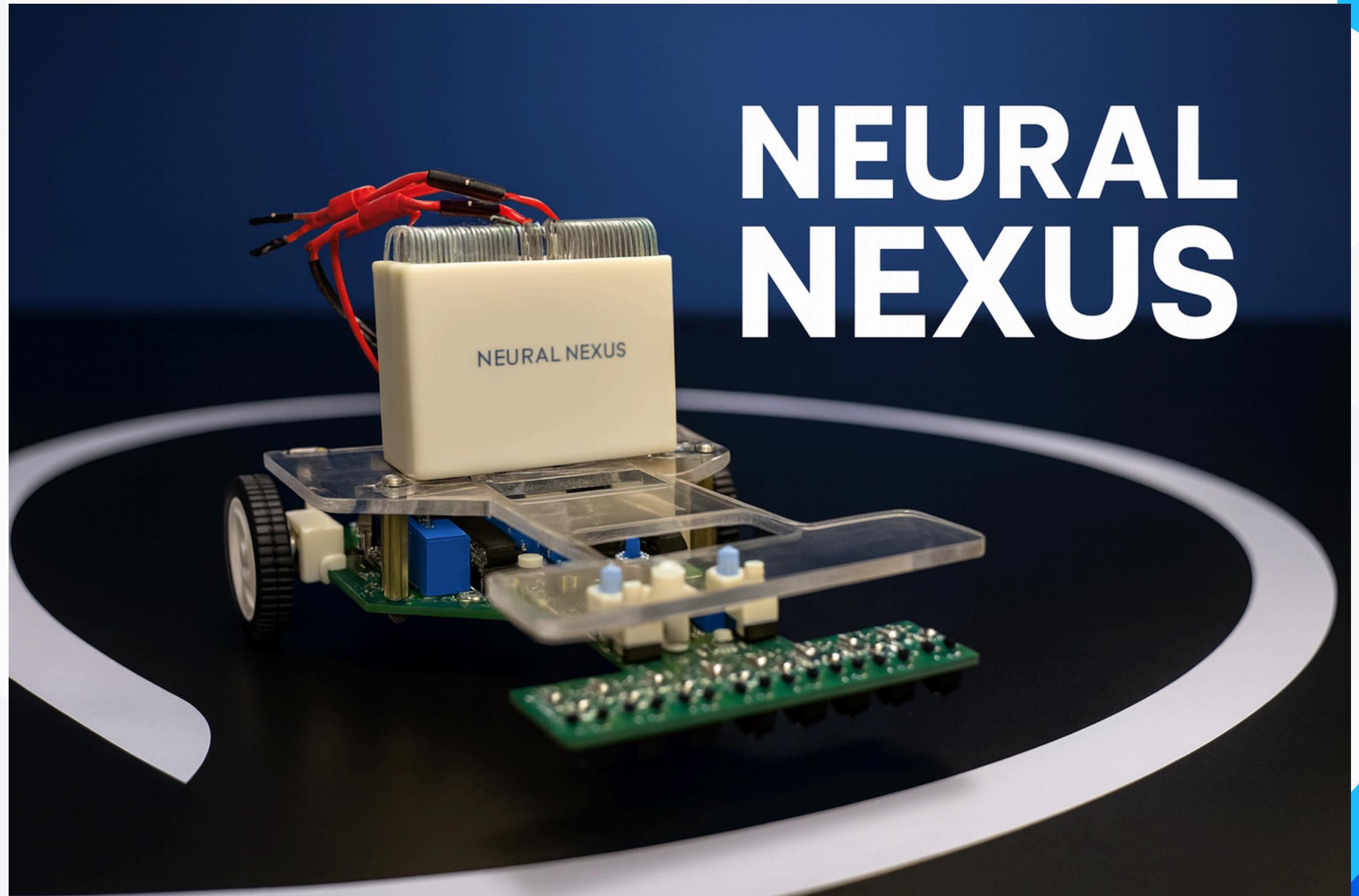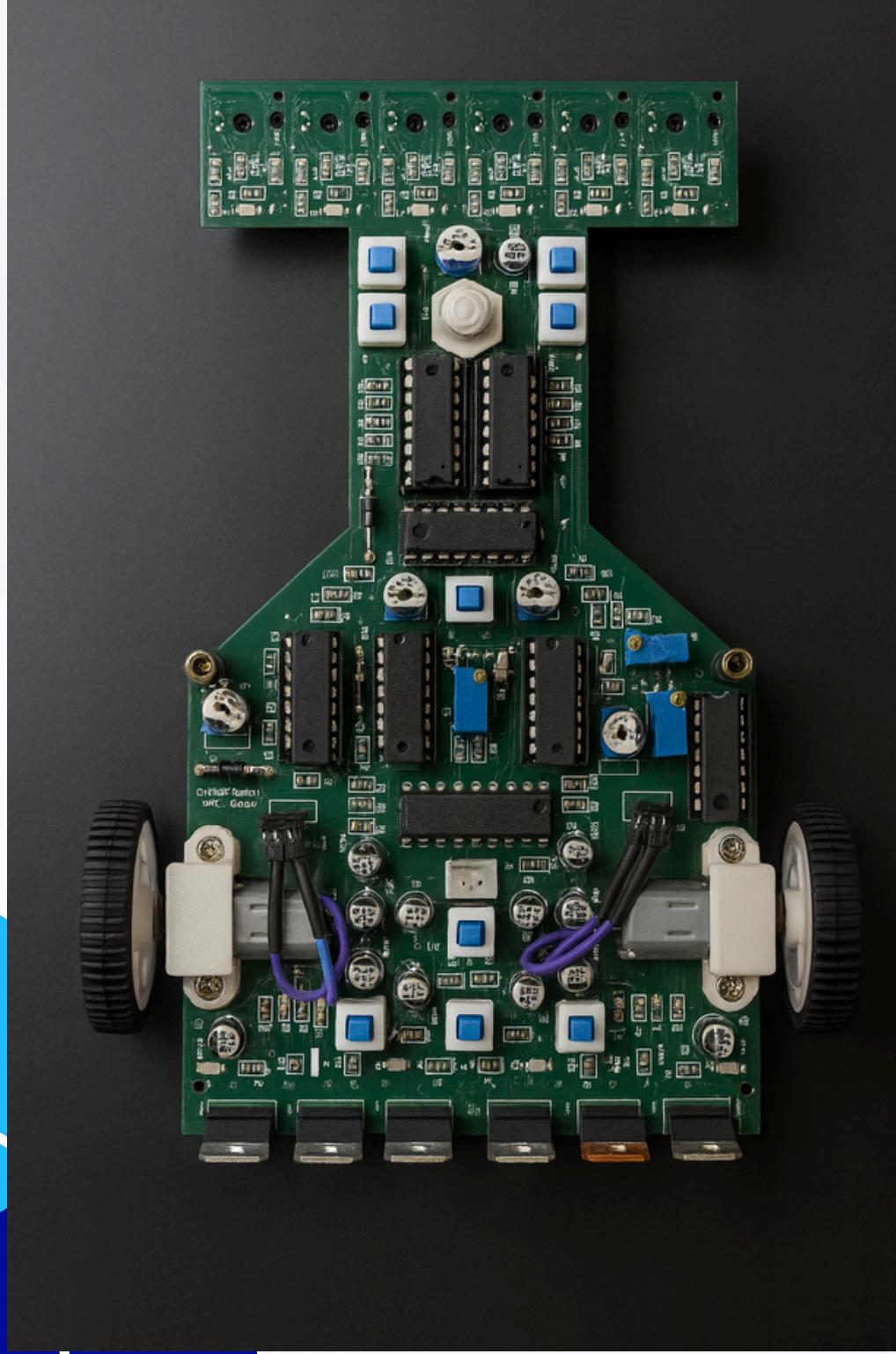

REFERENCES

Jojo. 2009. "Triangular Waveform Using Schmitt Trigger." **CircuitsToday**, September 22, 2009. <https://circuitstoday.com/triangular-waveform-using-schmitt-trigger>

National Instruments. 2025. "The PID Controller & Theory Explained." March 7, 2025. <https://www.ni.com/en/shop/labview/pid-theory-explained.html>

THANK YOU